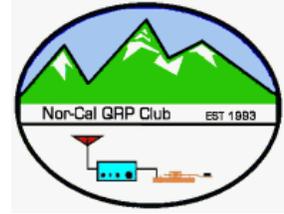


# NorCal QRP Club



[Print Friendly Version](#)

**Navigation**


- ◆ Home
- ◆ About NorCal
- Contact Us**
- ◆ Jim Cates Tribute
- ◆ Retired Kits ▶
- ◆ NorCal Manuals
- ◆ Members Projects ▶

## The NB6M Miniboats

By Wayne McFee NB6M  
Copyright 2000

Requests for an "outboard" version of the RF power amplifier used in the 5 Watt Mod for the SMK-1 led me to further research and experimentation which resulted in the amplifier circuit described in my article "A Mosfet QRP Gallon", published in the Fall, 2000 issue of QRPp, the journal of the NorCal QRP Club. The RF amplifier described utilized the cheap, readily available IFR510 Mosfet to produce 5 Watts of output with an input of from 1 to 1.5 Watts and was switched into and out of the antenna line from the QRP rig by a DPDT toggle switch.


Since that article was published, I have added several improvements to that basic RF Amplifier circuit. I call the new amplifier the "NB6M Miniboats". For those who are comfortable with building "Ugly Style" from a simple circuit, this project is a snap and the parts are all readily available. For those who would like the parts already gathered and the layout prepared for them, a kit is in the offing.

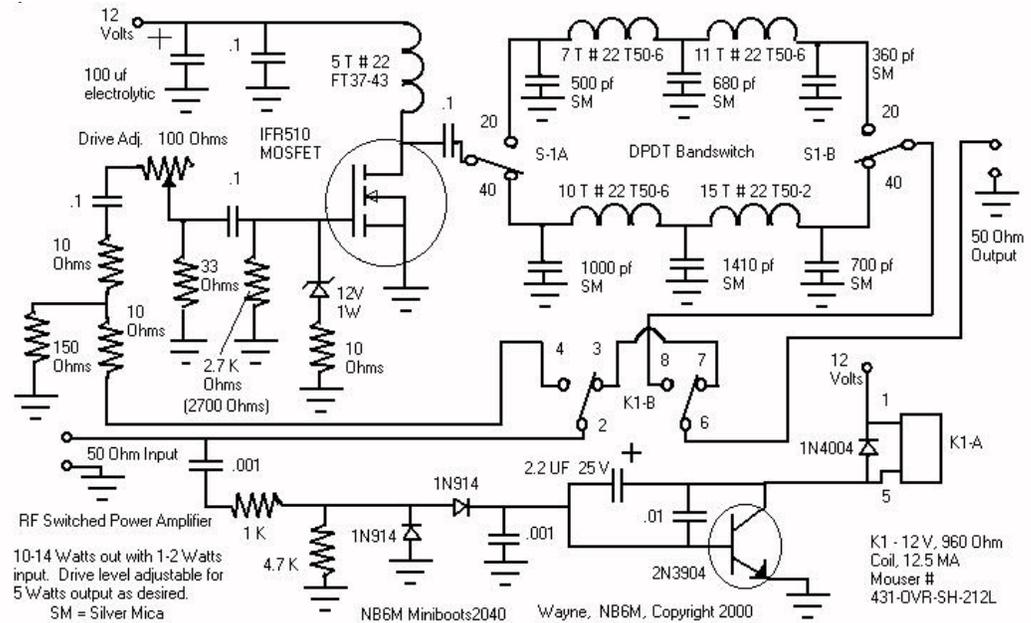

40/20 Meter version shown, with attenuator input for 1 to 2 Watts drive



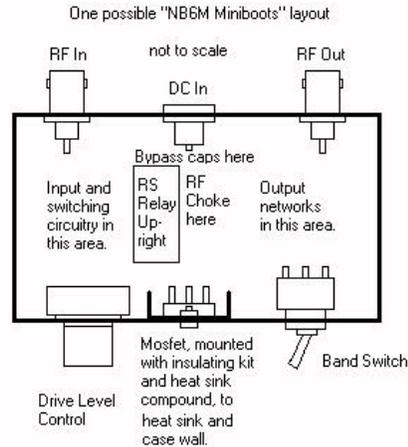None of the versions of the "Miniboats" built thus far have been laid out exactly the same, due to the "ugly" method of construction. However, that means that the individual builder can plan the layout so as to utilize any of a variety of enclosures. One possible layout is suggested in the attached drawing.



Wayne, NB6M Copyright 2000

A parts list and two circuits diagrams are provided, one with the resistive attenuator input to accept one to two Watts of drive, and another with the broadband transformer input to accept a drive level of three-quarter to one Watt.

If the broadband transformer input is used, insert a QRP SWR meter in the line between the driving rig and the amplifier and check the reflected power back to the rig. My antenna analyzer shows the amplifier with the transformer input to have an SWR of 1.3 to 1 or less from 1.8 Mhz up through 10 Mhz. At 14 Mhz, the SWR is 1.7 to 1. The number of turns on the primary of the broadband transformer can be adjusted as necessary in order to provide a better match.

The IRF510 will require heat sinking, and the Drain of the Mosfet must be insulated from ground. It is a good idea to use an Ohm-Meter to check for shorts from the Drain to ground before supplying DC power to the amplifier. The Miniboats could easily be built into an Altoids tin, if desired, making for a very small package.

The drive level adjustment pot can be either a trimpot, with a screwdriver access hole cut in the enclosure used, or can be a front panel mounted control with a knob. The choice is yours. Whichever style pot is used, the input circuit should be laid out so that short leads are used to connect the pot to the gate circuitry of the Mosfet. Also, if considerable operation is planned at Milliwatt levels, the pot should have a high enough wattage rating to be able to absorb its share of the RF input to the amplifier.

Two component value charts are provided for the output filter network.

Table 1 has component values for ten to fourteen Watts of output.

NB6M Miniboats					
	C-1	L-1	C-2	L-2	C-3
80 Meters	2000 pf	15 T # 22 T50-6	2700 pf	22 T # 22 T50-2	1462 pf
40 Meters	1000 pf	10 T # 22 T50-6	1462 pf	15 T # 22 T50-2	720 pf
30 Meters	680 pf	8 T # 22 T50-6	1000 pf	13 T # 22 T50-6	470 pf
20 Meters	500 pf	7 T # 22 T50-6	680 pf	11 T # 22 T50-6	360 pf
17 Meters	400 pf	6 T # 22 T68-6	550 pf	10 T # 22 T50-6	275 pf
15 Meters	330 pf	6 T # 22 T50-6	470 pf	8 T # 22 T68-2	240 pf
12 Meters	280 pf	5 T # 22 T50-2	400 pf	8 T # 22 T50-2	200 pf
10 Meters	250 pf	5 T # 22 T50-6	340 pf	8 T # 22 T50-6	180 pf

Table 1. 10-14 Watt output network component values

Wayne, NB6M

copyright 2000

TABLE 1

Table 2 has component values for a nominal 5 Watt output, should the builder desire to build the amplifier for use only up to the QRP Gallon level.

NB6M Miniboos					
	C-1	L-1	C-2	L-2	C-3
80 Meters	820 pf	21 T # 24 T50-2	1600 pf	25 T # 24 T50-2	910 pf
40 Meters	390 pf	16 T # 24 T37-2	820 pf	19 T # 24 T37-2	470 pf
30 Meters	270 pf	13 T # 24 T37-2	560 pf	16 T # 24 T37-2	330 pf
20 Meters	220 pf	11 T # 24 T37-2	390 pf	13 T # 24 T37-2	240 pf
17 Meters	180 pf	10 T # 24 T37-2	330 pf	14 T # 24 T37-6	180 pf
15 Meters	150 pf	9 T # 24 T37-2	270 pf	11 T # 24 T37-2	150 pf
12 Meters	135 pf	10 T # 24 T37-6	230 pf	10 T # 24 T37-2	135 pf
10 Meters	120 pf	9 T # 24 T37-6	220 pf	11 T # 24 T37-6	120 pf

Table 2. 5 Watt output network component values

Wayne, NB6M

copyright 2000

**TABLE 2**

At this point, component values are provided for the 17 Meter through 10 Meter ham bands for information only, as initial tests indicate that some circuit modification may be necessary to allow for satisfactory operation on the higher frequency bands. As stated, further testing is in progress.

An automatically switched, outboard RF Power Amplifier which allows for operation at power levels from Milliwatts to several Watts is a very useful addition to the QRP ham shack. Whether you decide to build the "NB6M Miniboos" for operation only at true QRP output levels, or for optional operation at low QRO levels as well, I am sure you will be more than satisfied with the results.

### Enjoy!

#### MiniBoos Parts List

.1 uf	4
.01 uf	1
.001 uf	2
2.2 uf Electrolytic	1
100 uf Electrolytic	1
100 Ohm trimpot or panel mounted pot, as desired	1
33 Ohm, 1 Watt	1
2.7 Kohm, 1 Watt	1
10 Ohm, 1 Watt	1
1 KOhm, 1 Watt	1
4.7 KOhm, 1 Watt	1
12 Volt, 1 Watt Zener Diode	1
1N914 (or 1N4148)	2
1N4004 Silicon Diode	1
2N3904 General Purpose Transistor (2N4401, etc)	1
IRF510 Mosfet	1
RF Choke, FT37-43 with 5 Turns # 22	1
12 Volt, DPDT Relay	
Mouser # 431-OVR-SH-212L or Radio Shack RS275-249A	1
RF Jacks, BNC Type	2
Power Connector	1
For resistive attenuator input	
10 Ohm, 1 Watt	2
150 Ohm, 1 Watt	1
For broadband transformer input	
FT37-43, Primary 6 Turns # 24, Secondary 4 Turns # 24	1
If two-band operation is desired, add	
DPDT Toggle Switch	1

If multiple-band operation is desired, add Rotary switch, dual contact, multiple-position as desired

For output filter component values, see Tables 1 and 2

Enclosure as desired.

---

Page last updated: 03/11/2019, 21:08:58  
Page Maintained by: [dean@alpinesoft.com](mailto:dean@alpinesoft.com)  
Copyright © 1993-2019, NorCal QRP Club, Inc. All rights Reserved.

---