

Figure 2: Simple biasing circuit is added to the Miniboosts design

board and a short length of hookup wire was connected between the lifted end of R7 and the junction of C20 and RV3, as shown in below in Figure 3.

The additional components needed for the biasing circuit and T/R switching could be added to the Miniboosts amp in a variety of ways, including making use of a small “daughter board”, which could be attached to the inside of the case. I chose to use the “Ugly” method, as will be shown later.

A Milliammeter was connected in series with the DC supply line, and the quiescent current set at 100 milliamps.

In tests conducted both off and on the air, while monitoring both quiescent current through the amplifier and heating of the Mosfet, it was found that, with just one TO-220 type aluminum heat sink bolted directly to the transistor, in the open air, the quiescent current remained below 150 milliamps during reasonable length transmit periods, and returned to the 100 milliamp level dur-

ing receive periods. This indicated that a larger heat sink might well keep device heating, and, therefore quiescent current, well under control.

Monitored audio quality of off the air tests indicated no distortion. All stations contacted in on-the-air testing were asked to make a critical report on audio quality, and all responded with favorable reports.

Once initial testing was done, Q3 and R13 were added to the circuit in order to have the bias circuit switched on and off for transmit and receive periods, respectively. By doing this, not only is current drain minimized, but cooling of the Mosfet is enhanced, by virtue of its not carrying 100 milliamps of quiescent current during receive periods, as shown in Figure 4.

Following the “Ugly” method of construction, the grounded ends of D1 and R4 were used as attachment points for the grounded end of RV3 and the grounded ends of C20 and D5. See Figure 5 on the next

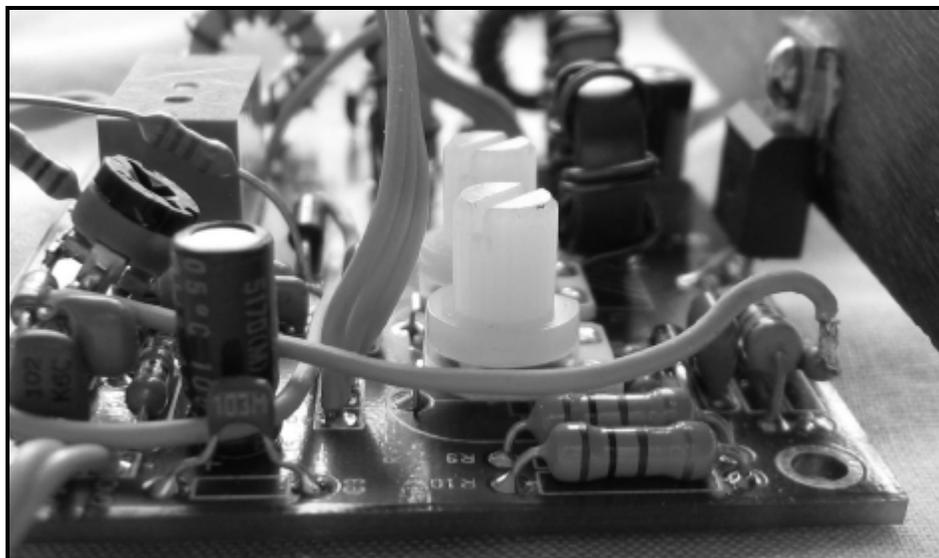


Figure 3: One end of R7 is lifted and connected by hookup wire to C20/RV3

page for clarification.

Because of the low current requirements of the Mosfet biasing circuit, all resistors used are ¼ watt units, and RV3 is a subminiature trimpot.

As seen in the initial picture of the SSB/CW modified Miniboosts, a relatively large heat sink was bolted directly to the metal tab of the IRF510. This was done to test the feasibility of operating the amplifier in PSK-31 mode.

This heat sink has a body that is .125” thick, is 1.75” high, over 4.0” wide, including its attachment wings, and with ten ribs which stand out .375” from the main body of the heat sink. This is a little bit of overkill, but what it did prove was that by using a large enough heat sink, the Miniboosts Amp with the SSB Mod could be used as a linear for PSK-31 operation. The Mosfet only got detectably warm during long transmission periods in that 100% duty cycle mode.

The entire SSB Modified Miniboosts circuit is shown in Figure 6.

As always, testing and modification will continue. If you choose to add this simple biasing circuit to your Miniboosts Amplifier, I recommend first adjusting the output level for no more than 5 Watts. You should also perform enough testing to be sure that the heat sink you are using is up to the task of keeping the Mosfet at a reasonable operating temperature. This will help ensure that your signal remains undistorted and the transistor is protected from destruction.

I am pleased with the experimental results so far! It shows that the Miniboosts can be a very useful addition to the QRP SSB voice and digital modes of operation as well as for CW. I hope your results will be as good as mine.

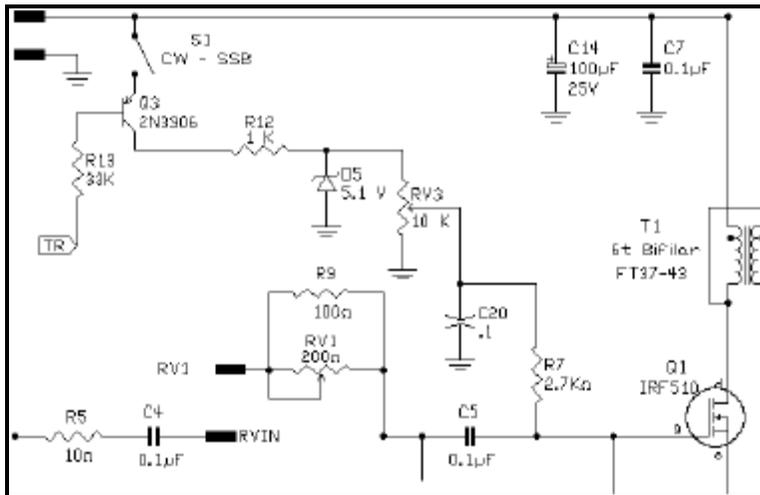


Figure 4: Q13, R3 and S1 added to allow switching bias circuit on/off during Tx/Rx periods

NOTES

1. Hayward, Wes, W7ZOI, *Experimental Methods in RF Design*
2. Hayward, Wes, W7ZOI, Lewallen, Roy, W7EL, DeMaw, Doug, W1FB, various publications
3. DeMaw, Doug, *W1FB's Design Notebook*
4. You may contact the author by email at NB6M@aol.com, or by postal mail at: 2379 Saint George Drive, Concord, CA 94520.
5. The original Miniboosts Amp Kit provides a full "QRP gallon" (5-Watt output) from a 750mW-to-1W input CW drive signal. It comes with BNC connectors, all board mounted parts and a high quality silk screened, solder masked, plated through hole pc board. All you have to add is the power connector of your choice and a case. See full kit details and ordering information on the AmQRP web site at <http://www.amqrp.org/kits/miniboosts/index.html>.



Figure 5: "Ugly" construction techniques shown here for D1, R4 and RV3. Also shown here is Q3 mounted by its emitter to the back of S1, with R12 connecting its collector to the junction of D5 and RV3, and with one lead of R13 shown connected to its base.


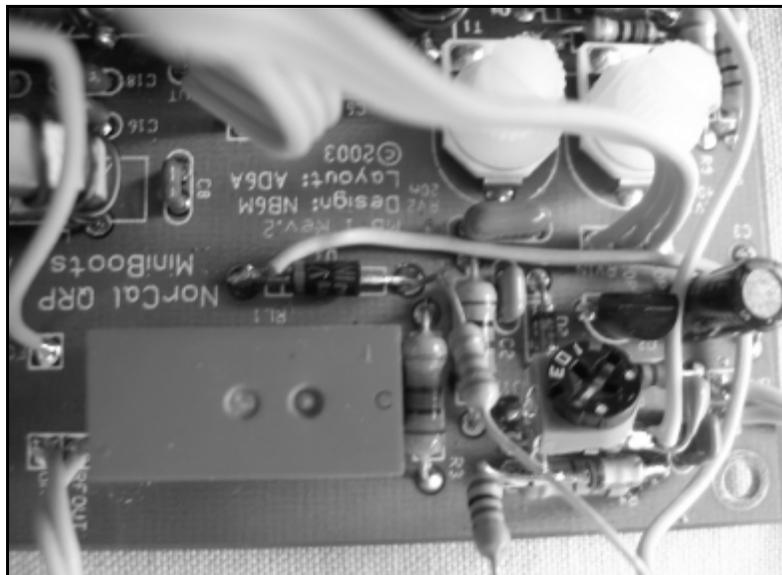


Figure 6: The cathode and anode of D3 were used as attachment points for the 12 Volt and T/R lines running to S1 and the base of Q3. This photo also gives another view of the attachment points of C20, the 0.1 cap in lower right, RV3, the 10 K trimpot, and D5, the silver diode below RV3. Also shown are R13, the 33K resistor connected from the anode of D3 to the base of Q3, and R12, which goes between the collector of Q3 and the junction of D5 and RV3.

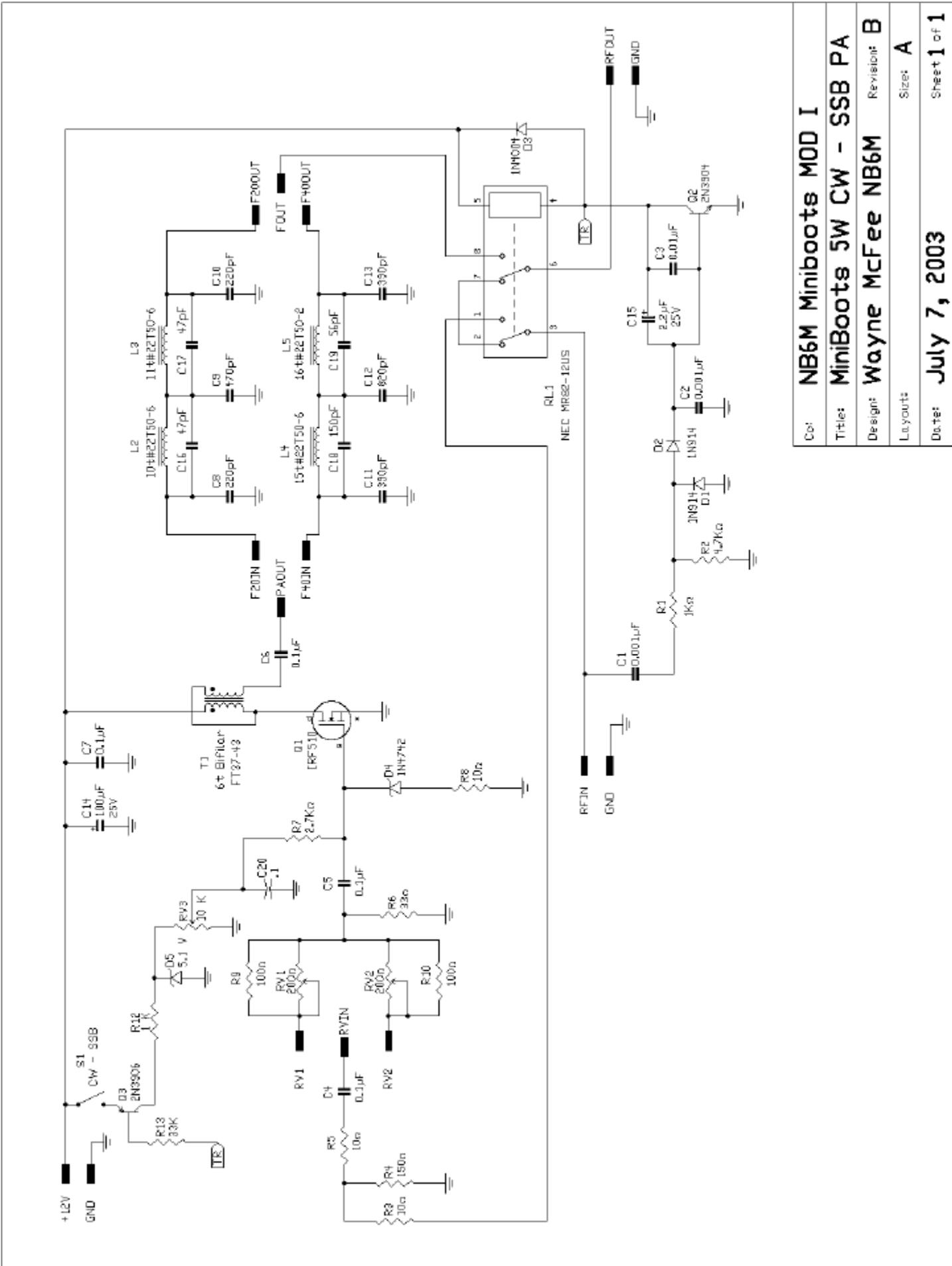

Co:	NB6M Miniboosts MOD I
Title:	MiniBoosts 5W CW - SSB PA
Design:	Wayne McFee NB6M Revision: B
Layout:	Size: A
Date:	July 7, 2003 Sheet 1 of 1